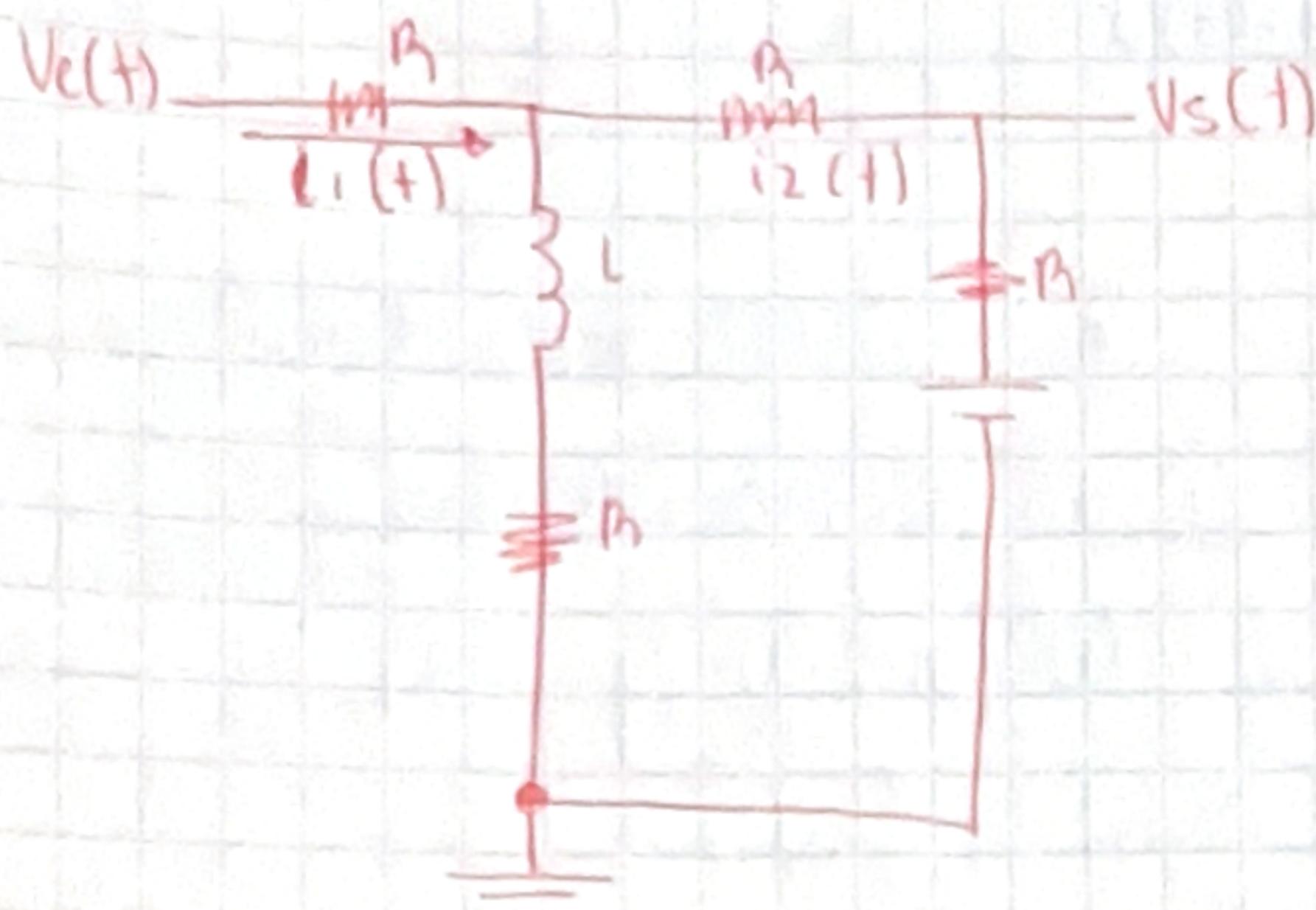


23-Sep 2025

Calculos



- Ecuaciones principales

$$V_e(t) = R_1 i_2(t) + L \frac{di_1(t)}{dt} - i_2(t) + R_2 [i_1(t) - i_2(t)]$$

$$\underline{L \frac{di_1(t) - i_2(t)}{dt}} + R_2 [i_1(t) - i_2(t)] = R_1 i_2(t) + R_2 i_2(t) + \frac{1}{C} \int i_2(t) dt$$

$$V_s(t) = R_1 i_2(t) + \frac{1}{C} \int i_2(t) dt$$


- Modelo de ecuaciones integro-diferenciales.

$$i_1(t) = V_e(t) - \underline{L \frac{di_1(t) - i_2(t)}{dt}} + R_2 i_2(t) \frac{1}{2R}$$

$$i_2(t) = \underline{[L \frac{di_1(t) - i_2(t)}{dt}]} + R_1 i_1(t) - \frac{1}{C} \int i_2(t) dt \frac{1}{3R}$$

$$V_s(t) = R_1 i_2(t) + \frac{1}{C} \int i_2(t) dt$$

Modelar ecuaciones simulink

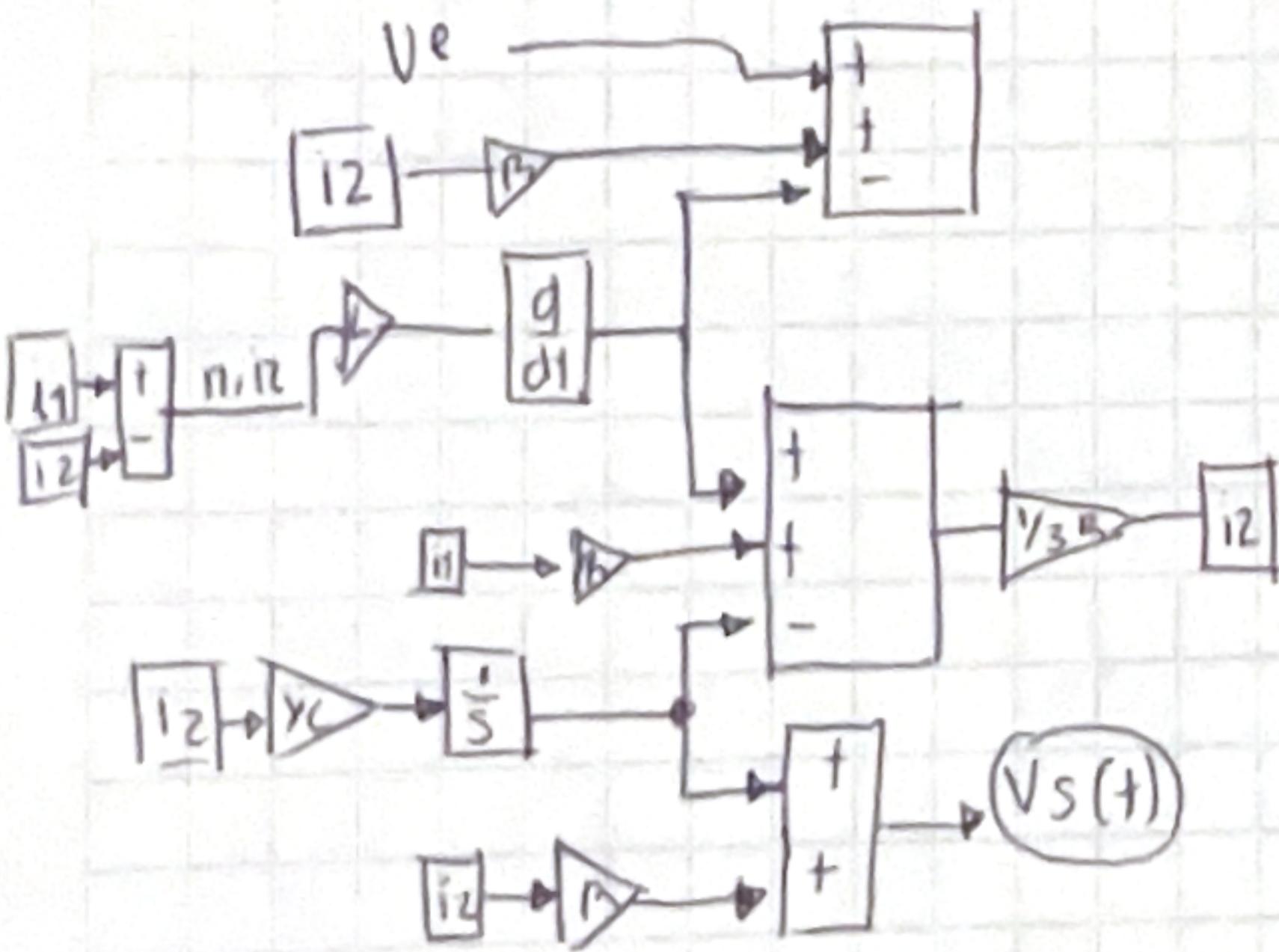

$$\bullet V_e(t) = R_1 i_1(t) + L \frac{di_1(t) - i_2(t)}{dt} + R_2 [i_1(t) + i_2(t)]$$

$$\underline{L \frac{i_1(t) - i_2(t)}{dt}} + R_2 [i_1(t) - i_2(t)] = R_1 i_2(t) + \frac{1}{C} \int i_2(t) dt$$

26. Sep. 2025

• Transformada de Laplace

$$V_e(s) = R I_1(s) + L S L I_1(s) - I_2(s)] + R [I_1(s) - I_2(s)] \\ L S [I_1(s) - I_2(s)] + R [I_1(s) - I_2(s)] = R I_2(s) + R I_2(s) + \frac{I_2(s)}{C S} \\ V_s(s) = R I_2(s) + I_2(s) \\ \frac{I_2(s)}{C S}$$

• Procedimiento algebraico

$$V_e(s) = R + L S + R) I_1(s) - (L S + R) I_2(s) \\ = (L S + 2 R) I_1(s) - (L S + R) I_2(s)$$

$$L S I_1(s) - L S I_2(s) + R I_1(s) - R I_2(s) = 2 R I_2(s) + I_2(s) \\ L S I_1(s) + R I_1(s) = 3 R I_2(s) + L S I_2(s) + \frac{I_2(s)}{C S}$$

$$(L S + R) I_1(s) = (3 R + L S + \frac{1}{C S}) I_2(s) \\ I_1(s) = \frac{3 C R S + (L S^2 + 1)}{C S (L S + R)} I_2(s) \\ I_2(s) = \frac{C L S^2 + 3 C R S + 1}{C S (L S + R)} I_2(s)$$

• Sustitución I_2

$$V_e(s) = \frac{(L S + 2 R) ((L)^2 + 3 (R s + 1)) I_1(s) - (L S + R) I_2(s)}{(S (L S + R)} \\ = \left[\frac{(L S + 2 R) (C L S^2 + 3 (R + 1)) - (S (L S + R) (L S + R)}{S (L S + R)} \right] I_2(s)$$

$$C L^2 S^3 + 3 C L R S^2 + L S + 2 (L R S^2 + 6 C R^2 S + 2 R) \\ - (L^2 S^3 - 2 C L R S^2 - C R^2 S)$$

$$V_e(s) = \frac{3 C L R S^2 + (5 C R^2 + L) S + 2 R}{(S (L S + R)}$$

$$V(s) = \frac{C R S + 1}{C S} I_2(s)$$

$$\frac{3 (L R S^2 + (5 C R^2 + L) S + 2 R)}{C S (L S + R)} I_2(s)$$

$$(C R S + 1)(L S + R) = C L R S^2 + C R^2 S + L S + R$$

$$V_s(s) = \frac{C L R S^2 + (C R^2 + L) S + R}{3 C L R S^2 + (5 C R^2 + L) S + 2 R}$$

$$\text{num}[(100 E-6) * (2.2 E-3) \times (4.7 E 3), (100 E-6) + (4.7 E 3)^{1/2} + 2.2 E-3, 4.7 E 3]$$

$$R = 4.7 \Omega \\ L = 2.2 \text{ mH} \\ C = 100 \mu F$$

Estabilidad en lazo abierto

- Calcular los polos de la función de transferencia

$$\frac{V_s(s)}{V_e(s)} = \frac{CLRS^2 + (CR^2 + L)s + R}{3CLRS^2 + (SCR^2 + L)s + 2R}$$

$$\text{den} = [3 + C + L + R, 5 + C + R + 2 + L, 2 + R]$$


$$L = \text{np.roots}(\text{den})$$

?

→ fprint : las raíces son: $\{L[0]\}$ y $\{L[1]\}$

El sistema presenta una respuesta:

estable y sobreamortiguada

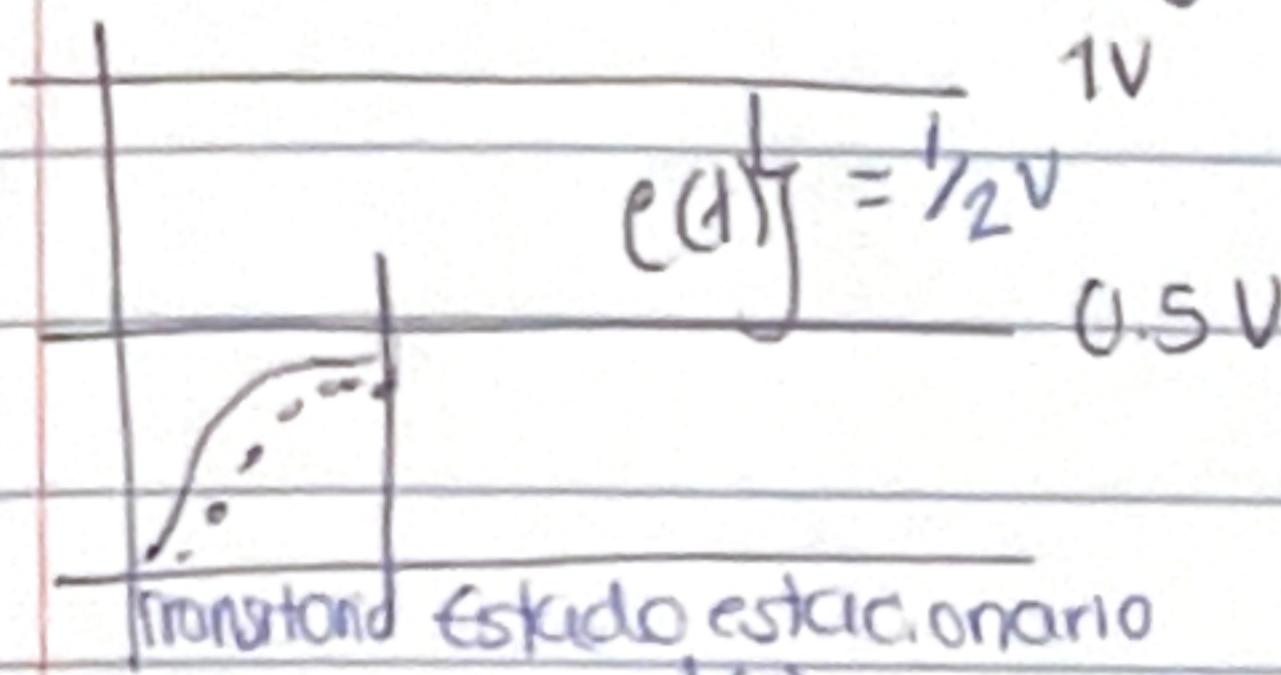

transitorio Estado estacionario

Error en estado estacionario $e(s)$

$$e(s) = \lim_{s \rightarrow 0} s V_e(s) \left[1 - \frac{V_s(s)}{V_e(s)} \right]$$

$$= \lim_{s \rightarrow 0} s \cdot \frac{1}{s} \left[1 - \frac{CLRS^2 + (CR^2 + L)s + R}{3CLRS^2 + (SCR^2 + L)s + 2R} \right]$$

$$= \frac{R}{2R}$$

$$V_e(t=1V)$$

$$e(t) = \frac{1}{2}V$$

$$V_e(s) = \frac{1}{s}$$